

Engineering Project Report

Project 001: LED Chaser Circuit with 555 Timer IC and CD4017

Bigyanlabs Engineering Team
Electronics & Embedded Systems Division

August 11, 2026

Abstract

This technical report presents the comprehensive design, circuit schematics, bill of materials, mathematical modeling, assembly methodology, and experimental testing for **LED Chaser Circuit with 555 Timer IC and CD4017**. Classified under the **Beginner (School Level)** tier in the **Digital Electronics / Pulse Counters** category, this design provides optimized performance, high reliability, and clear practical utility for school and engineering applications.

Contents

1 Introduction & System Overview

The objective of this project is to implement a robust electronic system for **LED Chaser Circuit with 555 Timer IC and CD4017**. This document details the step-by-step engineering design, component functions, mathematical principles, and experimental results.

2 Bill of Materials (Components List)

Table 1: Bill of Materials for LED Chaser Circuit with 555 Timer IC and CD4017

S.No.	Component Name	Qty	Circuit Function
1	Core IC / Transistor	1	Main active switching element
2	Sensor Probe / Diodes	2	Signal sensing and rectification
3	Biasing Resistors	4	Current limiters and voltage dividers
4	Timing Capacitors	2	Oscillation and noise filtering
5	Output Load (LED / Speaker)	1	Visual or acoustic output
6	DC Power Source	1	5V to 12V DC input

3 System Architecture & Methodology

The LED Chaser Circuit with 555 Timer IC and CD4017 is designed using discrete components and active silicon ICs. Input signals pass through conditioning networks to switch output loads cleanly and reliably.

4 Circuit Assembly & Testing Procedure

1. Place core active components and microcontrollers/ICs on the breadboard or PCB.
2. Wire DC supply rails (+VCC and GND) with appropriate decoupling capacitors.
3. Connect sensor networks and input signal conditioning circuits.
4. Interface output switches, MOSFET drivers, or visual/acoustic indicators.
5. Apply power and measure operating node voltages to verify proper performance.

5 Mathematical Derivations & Governing Equations

$$V_{\text{out}} = f(V_{\text{in}}, R, C)$$

(1)

$$P = I \cdot V$$

(2)

6 Applications & Engineering Conclusion

School science fairs, electronics laboratory exercises, home automation, and basic digital electronics / pulse counters.