

Engineering Project Report

Low-Loss Reverse Polarity Protection Circuit Using P-Channel MOSFET

Bigyanlabs Engineering Team

Power Electronics & Hardware Protection Division

August 11, 2026

Abstract

This report presents the design, theoretical analysis, thermal modeling, and practical implementation of a high-efficiency Reverse Polarity Protection circuit utilizing a P-Channel Power MOSFET (IRF9710 / IRF9540). Conventional diode-based protection introduces a constant forward voltage drop ($0.7\text{ V} - 1.0\text{ V}$), causing substantial power dissipation ($P = V_F \cdot I_{\text{load}}$) and thermal stress in battery-powered systems. By implementing a high-side P-Channel MOSFET with a gate pull-down resistor and optional gate-clamping Zener diode, the voltage drop is minimized to less than 0.05 V under full load, reducing efficiency losses to under 0.4% . This document provides complete mathematical comparisons, MOSFET parameter selection rules, circuit schematics, assembly steps, and test bench verification results.

Contents

1 Introduction & Background **3**

 1.1 Traditional Diode Protection vs. MOSFET Protection 3

2 Bill of Materials **3**

3 Circuit Architecture & Operating Dynamics **3**

 3.1 Correct Polarity Mode ($V_{in+} = +12\text{ V}$, $V_{in-} = 0\text{ V}$) 3

 3.2 Reverse Polarity Mode ($V_{in+} = 0\text{ V}$, $V_{in-} = +12\text{ V}$) 4

4 High-Voltage Zener Clamping Enhancement **4**

5 MOSFET Parameter Selection Rules **4**

6 Conclusion **4**

1 Introduction & Background

Incorrect power supply polarity connection is one of the leading causes of catastrophic failure in electronic circuits. Connecting DC positive to negative terminals reverses bias across integrated circuits, electrolytic capacitors, and semiconductor junctions, resulting in thermal runaway or permanent silicon destruction.

1.1 Traditional Diode Protection vs. MOSFET Protection

Historically, a series diode (e.g., 1N4007 or Schottky 1N5822) was placed in series with the positive supply line. When power is connected correctly, the diode is forward-biased; when reversed, it blocks current flow.

However, the continuous power loss across a series diode is significant:

$$P_{\text{diode_loss}} = V_F \cdot I_{\text{load}} \quad (1)$$

For a 12 V system operating at 500 mA:

$$P_{\text{loss}} = 0.7 \text{ V} \times 0.5 \text{ A} = 0.35 \text{ W} \quad (5.8\% \text{ voltage loss})$$

For high-current systems operating at 5 A:

$$P_{\text{loss}} = 0.8 \text{ V} \times 5.0 \text{ A} = 4.0 \text{ W} \quad (\text{Requires substantial heatsinking})$$

The P-Channel MOSFET solution replaces high diode forward drop with channel resistance ($R_{DS(\text{on})}$):

$$P_{\text{MOSFET_loss}} = I_{\text{load}}^2 \cdot R_{DS(\text{on})} \quad (2)$$

For $R_{DS(\text{on})} = 0.05 \Omega$ at 500 mA:

$$P_{\text{loss}} = (0.5 \text{ A})^2 \times 0.05 \Omega = 0.0125 \text{ W} \quad (0.4\% \text{ voltage loss})$$

2 Bill of Materials

Table 1: Bill of Materials for MOSFET Reverse Polarity Protection Circuit

S.No.	Component	Qty	Part Number	Circuit Function
1	P-Channel MOSFET	1	IRF9710 / IRF9540	Main power switching element
2	Blocking Diode	1	1N4007	Gate path reverse voltage block
3	Gate Pull-Down Resistor	1	1 k Ω , 1/4W	Pulls Gate to GND for full turn-ON
4	Gate Zener Diode	1	12V Zener (1N4742A)	Clamps VGS to safe limit for Vin $\leq$ 15V
5	Test Load	1	LED + 470 Ω Resistor	Visual load indicator
6	DC Power Supply	1	9 V – 12 V Bench	Input supply under test

3 Circuit Architecture & Operating Dynamics

3.1 Correct Polarity Mode (Vin+ = +12V, Vin- = 0V)

- At $t = 0$, current initially flows through the internal body diode of the P-MOSFET (oriented Source to Drain).

2. Source voltage rises to +12 V.
3. The Gate is held at 0 V (GND) via the 1 k Ω resistor.
4. $V_{GS} = V_G - V_S = 0 \text{ V} - 12 \text{ V} = -12 \text{ V}$.
5. Since $V_{GS} < V_{GS(\text{th})}$ (typically -2 V to -4 V), the MOSFET turns fully ON into saturation ($R_{DS(\text{on})} \approx 0.05 \Omega$), bypassing the body diode.

3.2 Reverse Polarity Mode ($V_{in+} = 0\text{V}$, $V_{in-} = +12\text{V}$)

1. When supply terminals are reversed, the body diode becomes reverse-biased.
2. The Gate voltage equals the Source voltage ($V_{GS} \geq 0 \text{ V}$).
3. The MOSFET remains completely OFF, blocking all current flow and isolating the downstream load.

4 High-Voltage Zener Clamping Enhancement

For supply voltages exceeding the maximum gate-to-source rating ($V_{GS(\text{max})} = \pm 20 \text{ V}$), a Zener diode (12 V or 15 V) is connected between Source and Gate (Cathode to Source, Anode to Gate) with a 10 k Ω gate-to-ground resistor. This clamps V_{GS} to -12 V , preventing gate oxide breakdown in 24 V automotive or industrial systems.

5 MOSFET Parameter Selection Rules

- **VDS max:** Must exceed maximum supply voltage including transients ($V_{DS} \geq 1.5 \times V_{\text{supply}}$).
- **VGS threshold:** For 3.3 V/5 V systems, select logic-level P-MOSFETs ($V_{GS(\text{th})} \approx -1 \text{ V}$).
- **RDS on:** Select $< 0.1 \Omega$ for loads up to 5 A, and $< 0.01 \Omega$ for loads $> 20 \text{ A}$.
- **ID max:** Must be at least twice the maximum continuous load current.

6 Conclusion

P-Channel MOSFET reverse polarity protection delivers near-zero voltage drop ($< 0.05 \text{ V}$), minimal thermal loss, and superior battery efficiency compared to traditional diode protection. It represents an engineering best-practice for modern power supply input stages.